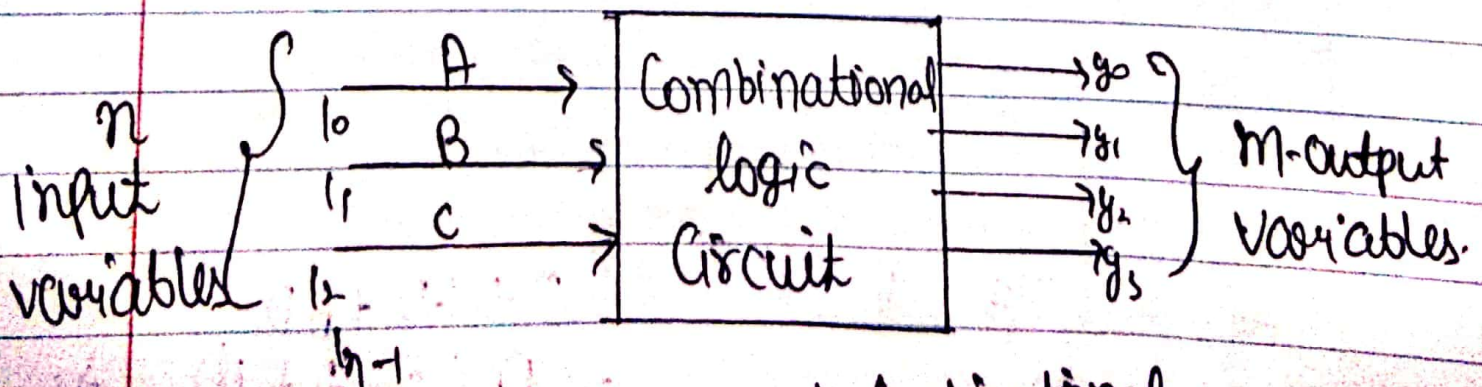


## Combinational Logic Circuits.

- The combinational logic gates are the circuits that contain different types of logic gates.
- A circuit in which different types of logic gates are combined is known as combinational logic gate.
- Combinational Circuits are Time Independent circuits, means the output at any time does not depend upon the previous unit, because there is no memory unit in these circuits.
- The input variables, logic gates and output variables are the basic components of combinational logic circuit.



(Basic diagram of combinational logic gates)

# *Ipwebdevelopers*

There are different types of combinational logic circuits such as Adder, Subtractor, Decoder, Encoder, Multiplexer, and De-multiplexer.

1. Adder
2. Subtractor.

① Adder:- Adders are the combinational logic (Arithmetic) circuits which are used for adding two or three binary bits.


## Types of Adder

- (i) Half Adder
- (ii) Full Adder
- (iii) Parallel Binary Adder.

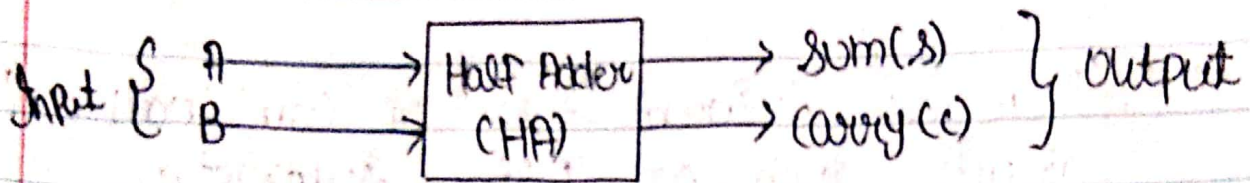(i) Half Adder:-

Half Adder adds two binary digits and produces two binary outputs called sum and carry.

It generates a sum (s) and carry (c) as output



Inputs:- In half Adder there are 2 inputs (A, B)

Output:- There are 2 outputs.

→ Sum (S)

→ Carry (C)

Truth Table:-

Input bits		Output	
A	B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

K-map for Half Adder:-

A/B	0	1	
0	0	1	→ $\bar{A}B$
1	1	0	

↓  
 $AB'$


A/B	0	1	
0	0	0	→ $AB$
1	0	1	

$$C = AB$$

$$S = \bar{A}B + A\bar{B}$$

$$= A\bar{A}B$$

## Logic Circuit

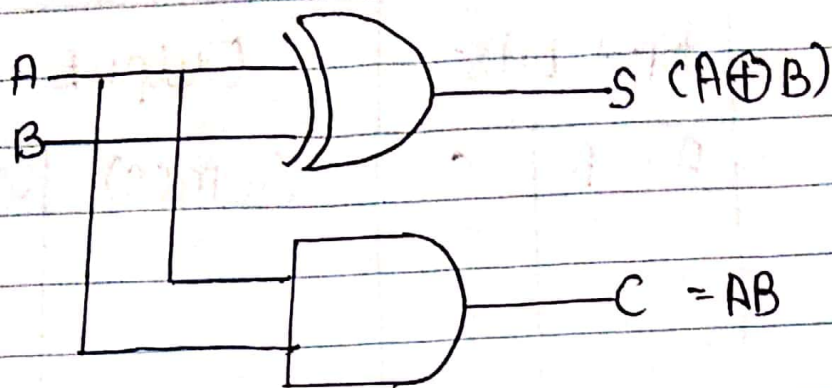


## (ii) Full Adder :-

Full Adder has three inputs A, B and additional carry-in ( $C_{in}$ ).

It is used to add three bits and generate two outputs, sum (S), carry (C).

## Block Diagram

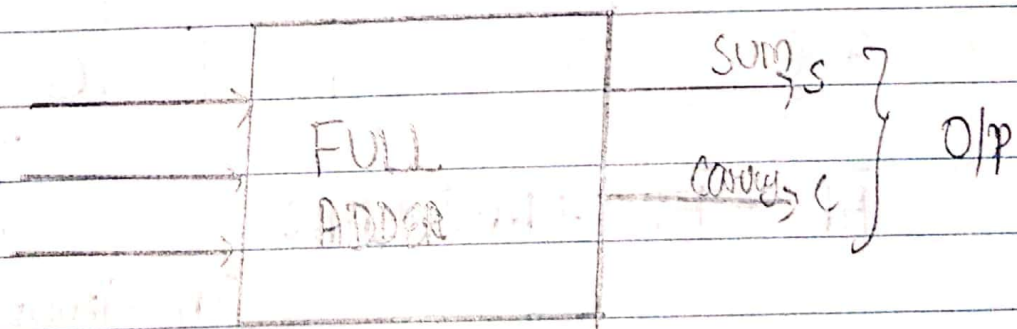

Inputs:- There are 3 inputs

Outputs:- There are 2 O/p.

## Truth Table

Input bits			Output	
A	B	C	Sum (S)	Carry (C <sub>o</sub> )
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## K-map for Full Adder

		(S)				(Carry C <sub>o</sub> )					
A \ BC		00	01	11	10	A \ BC		00	01	11	10
0			1		1	0			1		
1		1		1		1		1	1	1	

$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

In Group I (G<sub>I</sub>)

A	0, 1
B	1, 1
C	1, 1 = BC

Group-II

A	1,1
B	0,1
C	1,1

value change  
 $= AC$

Group-III)

A	1,1
B	1,1
C	0,1

$= AB$

$$\text{Carry} = BC + AC + AB$$


$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$= \bar{A}[\bar{B}C + B\bar{C}] + A[\bar{B}\bar{C} + BC]$$

$$= \bar{A}[B \oplus C] + A[B \odot C]$$

$$S = A \oplus B \oplus C$$

$$\text{Carry} = AB + BC + AC$$

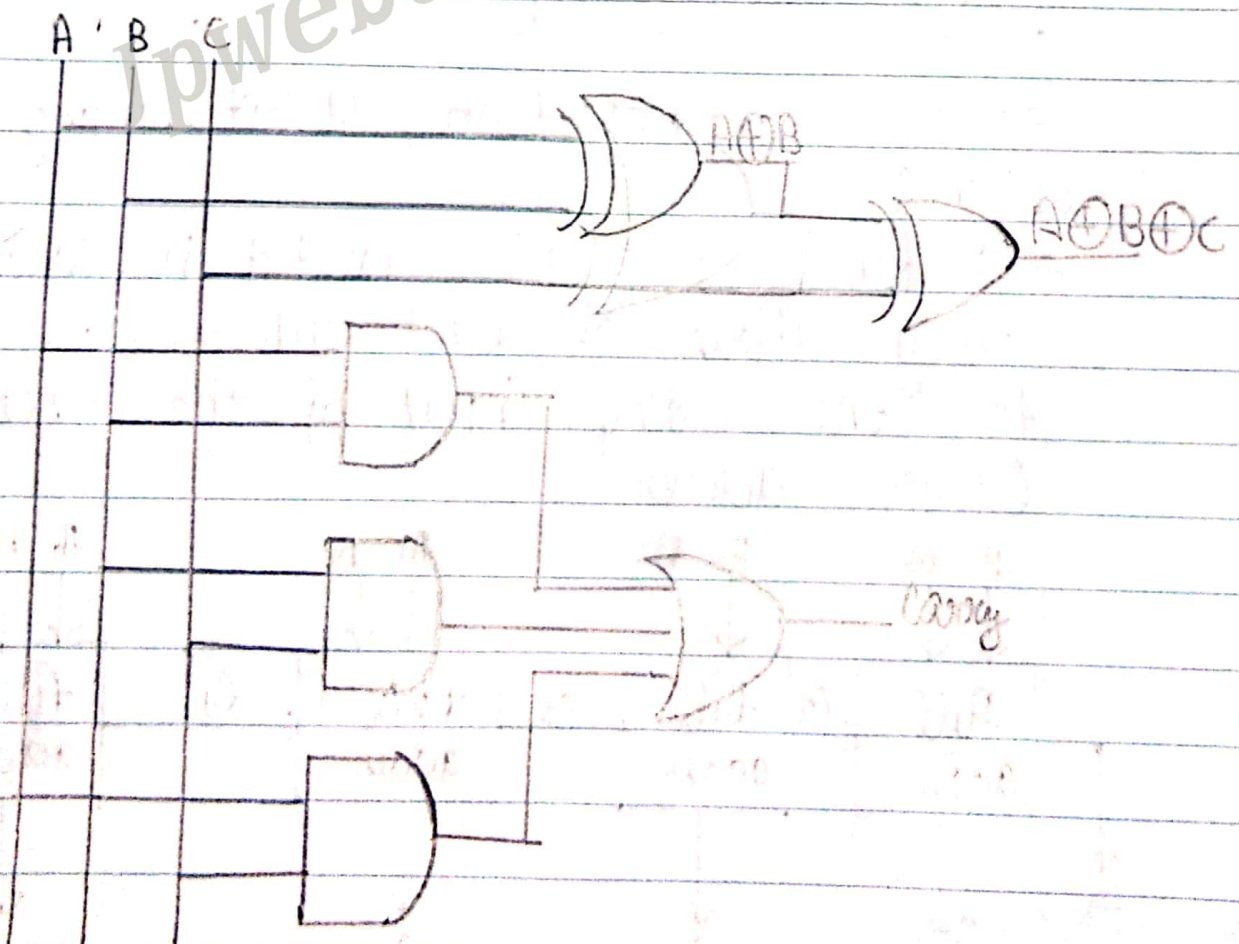

### (iii) Parallel Binary Adder :-

Parallel Binary Adder is a digital circuit which add two binary numbers of any length.


In this addition of more than 1 bit is carried out.

The addition of multibit numbers can be performed using several full adder.

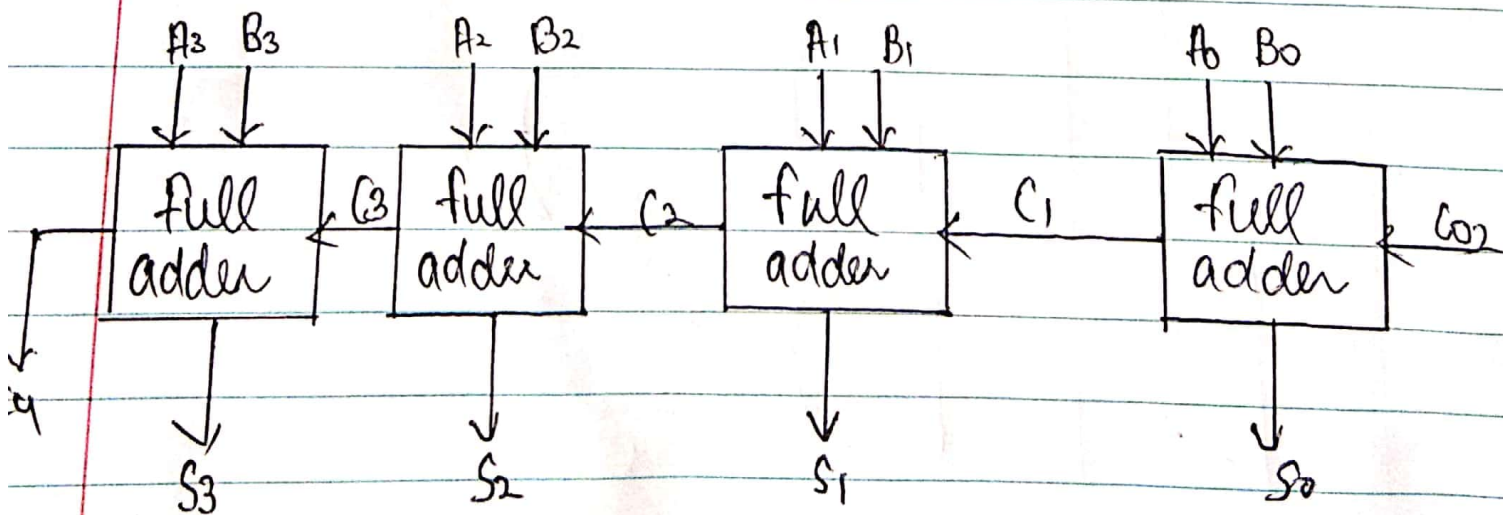
#### 4-bit Parallel adder / Ripple adder.

→ which can add two, 4 bit binary number.

→ 4 full adder are connected in cascade carry output of each adder is connected to the carry input of the next high order adder.



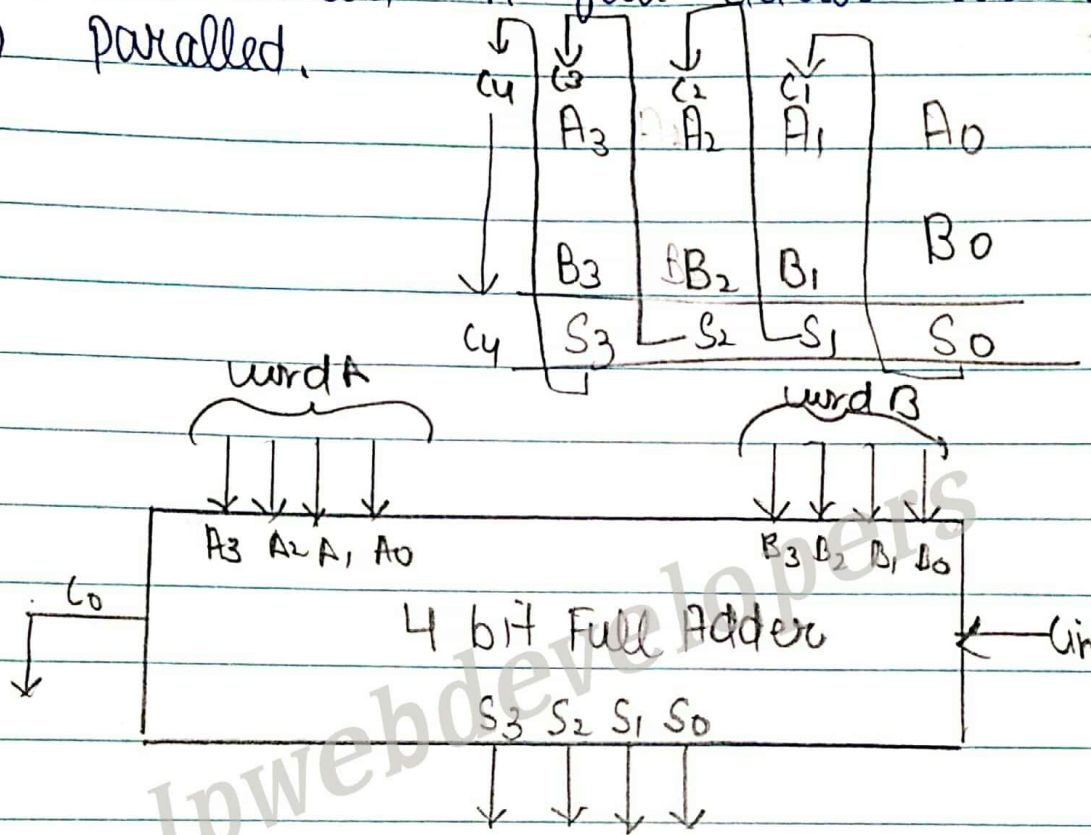→ So if want to add two, n-bits numbers then we need n- full adder arranged in parallel.



Download handwritten notes :-  
[jpwebdevelopers.in](http://jpwebdevelopers.in)

## (2) Subtractor:-

Subtractors are the combinational circuit which are used for subtracting two or three bits

- It is opposite of the Binary Adder.
- It subtracts two binary numbers from each other.
- The output is (i) Difference  
(ii) Borrow
- Binary subtraction of two bits

$$(i) \quad 0 - 0 \rightarrow 0 (D) \\ \rightarrow \text{Borrow is not required,}$$

$$(ii) \quad 1 - 0 \rightarrow 1 (D) \\ \rightarrow \text{Borrow is not required}$$

$$(iii) \quad 1 - 1 \rightarrow 0 (D) \\ \rightarrow \text{Borrow is not required}$$

$$(iv) \quad 0 - 1 \rightarrow 1 \\ \rightarrow \text{Borrow (1)}$$

→ There are two basic subtractors circuits are:-


- (i) Half Subtractor
- (ii) Full Subtractor.

(i) Half Subtractor:- A Half Subtractor is a combinational logic circuit that subtracts the two input bits.

Input:- There are 2 input in Half Subtractor.

Output:- There are 2 output in Half Subtractor

\* Block Diagram:-

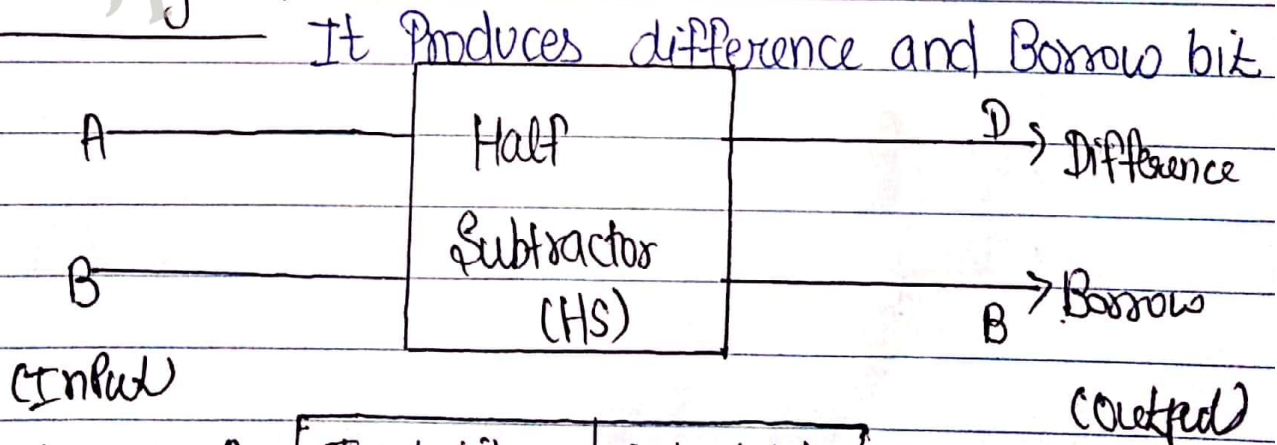

\* Truth Table:-

Input bits		Output bits	
A	B	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

## \* K-Map Representation

(Difference) (D)

A/B	0	1
0	0	1 → $\bar{A}B$
1	1 → $AB$	0

Borrow (B)


A/B	0	1
0	0	1 → $\bar{A}B$
1	0	0

$$D = \bar{A}B + AB$$

$$(A \oplus B)$$

$$B = \bar{A}B$$

## \* Logic Circuit

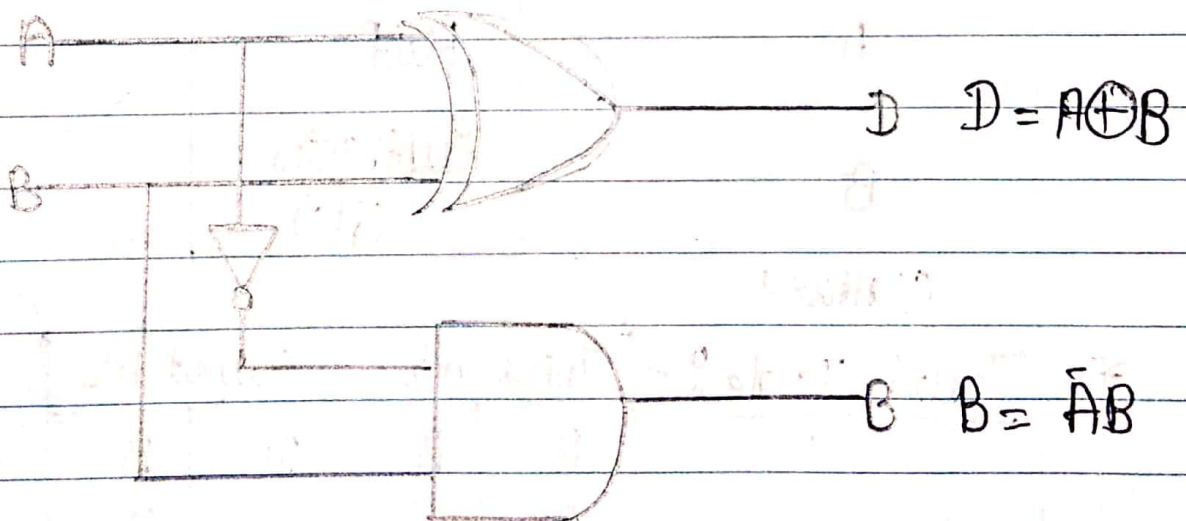


$$D = A \oplus B$$

$$B = \bar{A}B$$

## (ii) Full Subtractor

- A full Subtractor is a combinational circuit that are used to subtract three input bits and produces difference (D) and Borrow (B) at the output.
- It has three inputs, one additional Bin input:

\* Block Diagram:-

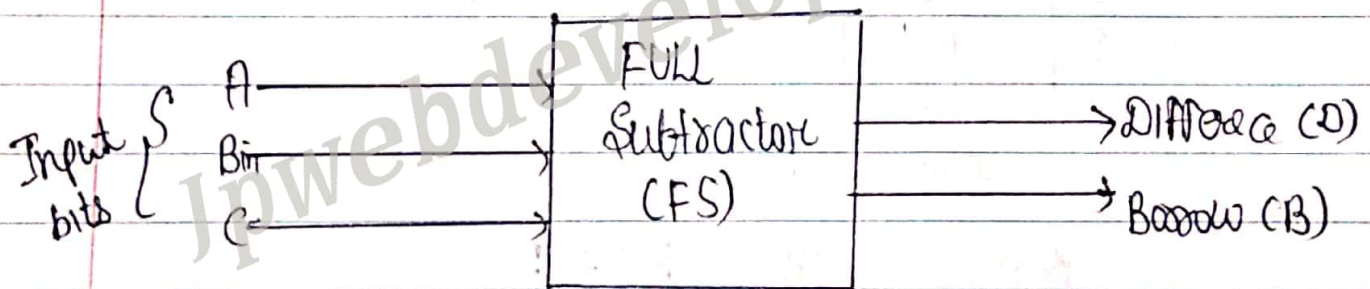

Inputs:- There are 3 inputs A, Bin, C.

Outputs:- There are 2 outputs (i) Difference (D) (ii) Borrow (B)

\* Truth Table:-

Input bits			Output bits	
A	B	C	(D) Difference	(B) Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

## \* K-Map Representation

Difference

	A \ BC	00	01	11	10
0		0	1	0	1
1		1	0	1	0

$$\begin{aligned} \text{Difference (Q)} &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\ &= A \oplus B \oplus C \end{aligned}$$

Borrow :-

	A \ BC	00	01	11	10
0		0	1	1	1
1		0	1	1	0

Group I (circled 1s in row 0)  
Group II (circled 1s in row 1)  
Group III (circled 1s in column 1)

$$\text{Borrow} = \bar{A}B + BC + \bar{A}C$$

Logic Diagram :-

